

PROBLEM SHEET 4

ANSWERS

1. a) $320 \text{ k}\Omega$; b) $16 \text{ k}\Omega$; c) 800Ω ; d) 16Ω
2. a) $40 \text{ k}\Omega$; b) $2 \text{ k}\Omega$; c) 50Ω ; d) 0.8Ω
3. a) 63Ω ; b) $1.3 \text{ k}\Omega$; c) $25 \text{ k}\Omega$; d) $1.3 \text{ M}\Omega$
4. a) 250Ω ; b) $7.5 \text{ k}\Omega$; c) $63 \text{ k}\Omega$
5. a) $X_C = 400 \Omega$; $X_L = 1 \text{ k}\Omega$; $X = 600 \Omega$; $Z = 1 \text{ k}\Omega$; $\varphi = 37^0$, voltage leads current
b) $X_C = 880 \Omega$; $X_L = 230 \Omega$; $X = 650 \Omega$; $Z = 720 \Omega$; $\varphi = 65^0$, voltage lags current