

## PROBLEM SHEET 2

## Capacitance and inductance in a d.c. circuit

1. A  $100\ \mu\text{F}$  capacitor is connected in series with an  $800\ \Omega$  resistor. The combination is connected suddenly to a  $100\ \text{V}$  d.c. supply. Determine:
  - a) The time constant of the circuit;
  - b) The initial rate of rise of the potential difference across the capacitor;
  - c) The initial charging current;
  - d) The ultimate charge in the capacitor;
  - e) The ultimate energy stored in the capacitor.
2. A  $2\ \mu\text{F}$  capacitor is connected in series with a  $2\ \text{M}\Omega$  resistor to a d.c. supply of  $100\ \text{V}$ . The capacitor is initially uncharged.
  - a) Plot a current-time graph using the graph paper;
  - b) Calculate the current flowing in the circuit at the end of an interval of  $4\ \text{sec}$  from the start.
  - c) Calculate the energy stored in the capacitor at the end of an interval of  $4\ \text{sec}$  from the start.
3. A large electromagnet is wound with  $1000$  turns. A current of  $2\ \text{A}$  produces a flux of  $0.03\ \text{Wb}$  through each turn of the coil.
  - a) Calculate the inductance of the electromagnet;
  - b) If the current in the coil is reduced from  $2\ \text{A}$  to zero in  $0.1\ \text{s}$ , what average EMF will be induced in the coil?
4. A coil wound with  $600$  turns has a resistance of  $2\ \Omega$ . It is found that a current of  $3\ \text{A}$  produces a flux of  $500\ \mu\text{Wb}$  through each turn. Calculate:
  - a) The inductance of the coil;
  - b) The time constant of the circuit;
  - c) The average EMF induced in the coil when the current is reversed within  $0.3\ \text{s}$ .
5. **ASSIGNMENT.** A coil having a resistance of  $25\ \Omega$  and an inductance of  $2.5\ \text{H}$  is connected across a  $50\ \text{V}$  d.c. supply. Plot the graph of the current as a function of time using the graph paper. Determine **graphically**:
  - a) The initial rate of the growth of the current;
  - b) The value of the current after  $0.15\ \text{s}$ ;
  - c) The time required for the current to grow to  $1.8\ \text{A}$ .