

PROBLEM SHEET 4

Elementary a.c. circuits

1. Determine capacitive reactance X_C for a capacitor $C = 10$ nF at frequencies:
a) $f = 50$ Hz; b) $f = 1000$ Hz; c) $f = 20$ kHz; d) $f = 1$ MHz.
2. Determine capacitive reactance X_C at frequency $f = 4$ kHz for a capacitor:
a) $C = 1000$ pF; b) $C = 20$ nF; c) $C = 0.8$ μ F; d) $C = 50$ μ F.
3. Determine inductive reactance X_L for a coil $L = 0.2$ H at frequencies:
a) $f = 50$ Hz; b) $f = 1000$ Hz; c) $f = 20$ kHz; d) $f = 1$ MHz.
4. Determine inductive reactance X_L at frequency $f = 4$ kHz for a coil:
a) $L = 10$ mH; b) $L = 300$ mH; c) $L = 2.5$ H.
5. A circuit consists of a resistor R , a capacitor C and a coil L connected in series. Determine capacitive reactance X_C , inductive reactance X_L , total reactance X , impedance Z of the circuit and phase difference φ between voltage and current if:
a) $R = 800$ Ω , $C = 2$ μ F, $L = 0.8$ H and angular frequency $\omega = 1260$ rad/sec;
b) $R = 300$ Ω , $C = 1.5$ μ F, $L = 0.3$ H and frequency $f = 120$ Hz.