

PROBLEM SHEET 8

Frequency effects

1. Determine the gain in decibels if the output voltage is larger than the input voltage:
 - a) 2 times; b) 3.16 times; c) 15 times; d) 20 times; e) 31.6 times; f) 80 times; g) 100 times; h) 316 times; i) 1000 times; j) 2000 times; k) 3162 times; l) 10000 times.
2. Determine the gain in decibels if the output voltage is smaller than the input voltage:
 - a) 2 times; b) 3.1 times; c) 15 times; d) 20 times; e) 31 times; f) 80 times; g) 100 times; h) 310 times; i) 1000 times; j) 2000 times; k) 3100 times; l) 10000 times.
3. Determine the cut-off frequency for a CR low-pass filter if:
 - a) $C = 0.01 \mu\text{F}$, $R = 1 \text{ k}\Omega$;
 - b) $C = 0.1 \mu\text{F}$, $R = 1 \text{ k}\Omega$;
 - c) $C = 0.2 \mu\text{F}$, $R = 20 \text{ k}\Omega$;
4. Determine the cut-off frequency for a LR high-pass filter if:
 - d) $L = 0.01 \text{ H}$, $R = 1 \text{ k}\Omega$;
 - e) $L = 0.1 \text{ H}$, $R = 1 \text{ k}\Omega$;
 - f) $L = 0.5 \text{ H}$, $R = 20 \text{ k}\Omega$;
5. **ASSIGNMENT.** In an LCR band-pass filter, $L = 40 \text{ mH}$, $C = 0.02 \mu\text{F}$ and $R = 150 \Omega$. Determine the resonant frequency, the Q-factor and the band width for this filter. The filter is connected to a 1 V a.c. voltage source at the resonant frequency. Find the voltage across the coil, across the capacitor and across the resistor in this case.
6. **ASSIGNMENT.** Show that both for a CR low-pass filter and for LR high-pass filter, the cut-off frequency $f_c = \frac{1}{2\pi\tau}$ where τ is the time constant of a CR or LR circuit respectively.
7. Using MATLAB, obtain a plot of the response as a function of frequency for an LCR band-pass filter with $L = 25 \text{ mH}$ and $C = 0.01 \mu\text{F}$. Use the frequency range from 1 to 20000 Hz and the resistance values of 100, 200, 500 and 1000 Ω .
8. Using MATLAB, obtain a plot of the response as a function of frequency for a CR low-pass filter with $R = 500 \Omega$ and $C = 1 \mu\text{F}$. Use the frequency range from 1 to 100000 Hz. Make the plot in a) a semilog scale (frequency - logarithmic, response - linear) and b) loglog scale (both frequency and response - logarithmic).

9. (*) Determine the phase difference between the input and output voltages:
- 1) For a CR low-pass filter at frequencies: a) cut-off frequency f_c ; b) $100 \times f_c$; c) $0.01 \times f_c$.
 - 2) For a LR high-pass filter at frequencies: a) cut-off frequency f_c ; b) $100 \times f_c$; c) $0.01 \times f_c$.
 - 3) For a LCR band-pass filter at frequencies: a) resonant frequency; b) cut-off frequencies f_1 and f_2 ; c) $100 \times f_2$; d) $0.01 \times f_1$.

You may choose any values of C , L and R

10. (*) Using MATLAB, obtain a plot of the phase difference between the input and output voltages as a function of frequency

- 1) For a CR low-pass filter
- 2) For a LR high-pass filter
- 3) For a LCR band-pass filter
- 4) For a LCR band-stop filter

You may choose any values of C , L and R