

PROBLEM SHEET 9

General theorems

1. **ASSIGNMENT.** Explain in your own words why the superposition theorem and the Thevenin's theorem are not true for non-linear circuits, i.e. containing diodes or transistors. Provide examples.
2. Using the superposition theorem, determine the current in the inductance for a circuit shown in Fig. 1. Assume that the voltage source (1) leads the voltage source (2) by 30° .
3. For a circuit on page 5 of the handouts, assume that it is connected to a source of 24 V a.c. with negligible internal resistance, R_1 is a capacitor of reactance 14Ω and R_4 is an inductance of reactance 24Ω . Using complex notations, find the current I_5 in the resistor R_5 and the voltage U_{AB} .

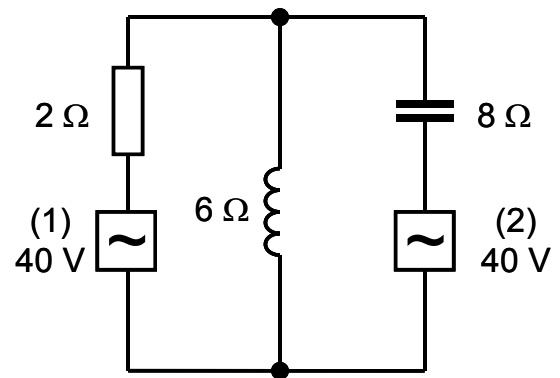


Figure 1.