
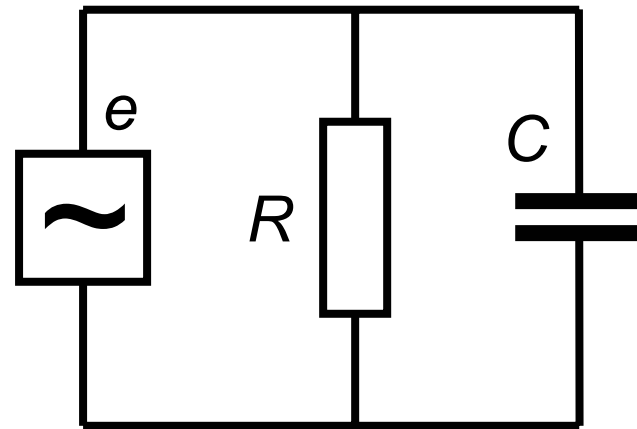


## 6. PARALLEL A.C. CIRCUITS
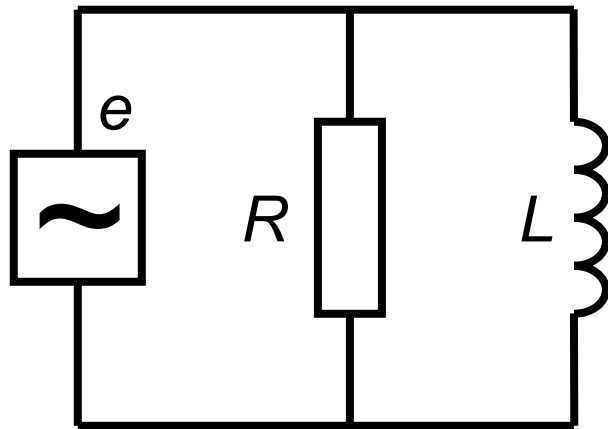
### Main things to learn

- Analysis of parallel a.c. circuits
- Active and reactive current
- Admittance and susceptance
- Power factor

Common way of connecting loads to the power supply is **in parallel**



*CR* or *LR* circuits in parallel. How to analyse them using phasor diagrams?


For series circuits, it was reasonable to take **current as a reference quantity**

However, in parallel circuits the voltage is the same across each element

Therefore, voltage is the most reasonable choice for reference

**It is common to use the voltage from the power supply as reference**
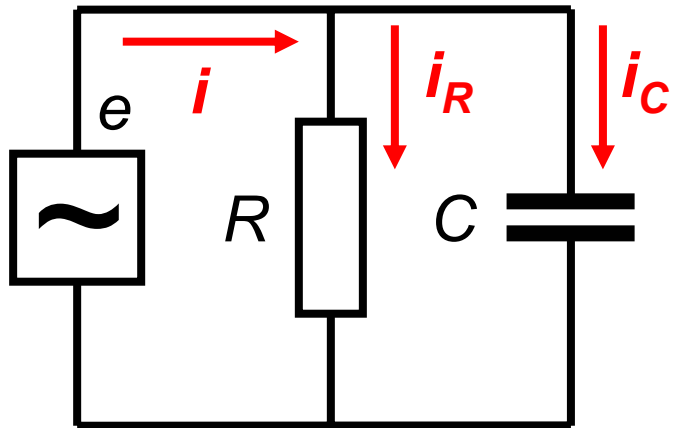
# PHASOR DIAGRAM FOR A **CR** CIRCUIT IN PARALLEL



$$I_R = U/R : i_R \text{ in-phase with } u$$

$$I_C = U/X_C : i_C \text{ leads } u \text{ by } \pi/2, X_C = 1/\omega C$$


**Phase:**

The total current  $i$  leads voltage  $u$   
(like for a series  $CR$  circuit)

$$\varphi = \tan^{-1} \frac{I_C}{I_R} = \tan^{-1} \frac{R}{X_C} = \tan^{-1} \left( \frac{\text{resistance}}{\text{reactance}} \right)$$

$$\underline{i} = \underline{i}_R + \underline{i}_C$$

**Voltage  $u$  - reference**

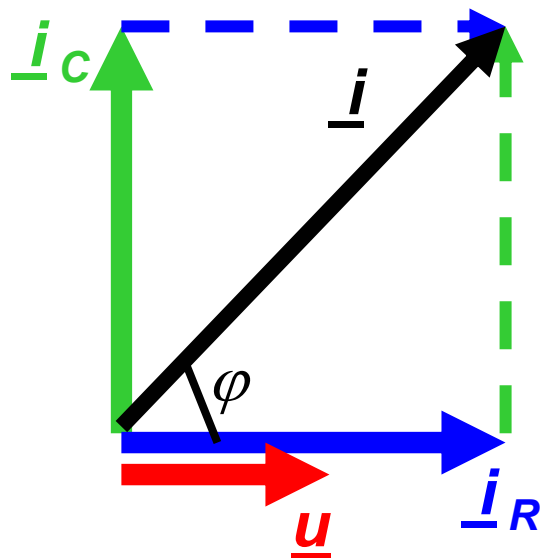


**Amplitude:**

$$I = \sqrt{I_C^2 + I_R^2} = U \sqrt{\frac{1}{X_C^2} + \frac{1}{R^2}} = \frac{U}{Z}$$

**Impedance:**

$$\frac{1}{Z} = \sqrt{\frac{1}{X_C^2} + \frac{1}{R^2}} = \sqrt{(\omega C)^2 + \frac{1}{R^2}}$$
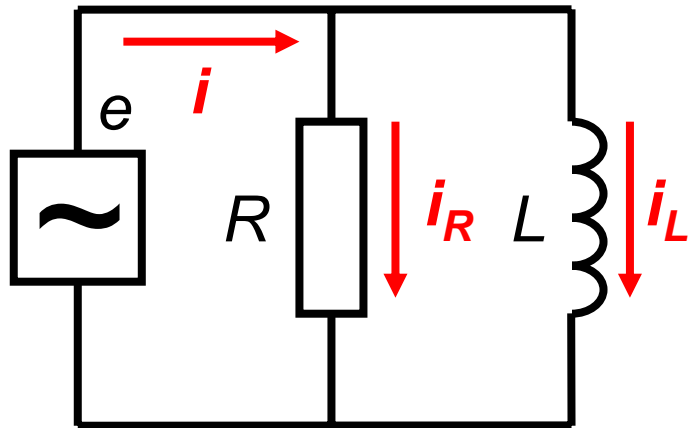
# PHASOR DIAGRAM FOR AN $LR$ CIRCUIT IN PARALLEL



$$I_R = U/R : i_R \text{ in-phase with } u$$

$$I_C = U/X_L : i_L \text{ lags } u \text{ by } \pi/2, X_L = \omega L$$

**Phase:**

The total current  $i$  lags voltage  $u$   
(like for a series  $LR$  circuit)

$$\underline{i} = \underline{i}_R + \underline{i}_L$$

Voltage  $u$  - reference


$$\varphi = -\tan^{-1} \frac{I_L}{I_R} = -\tan^{-1} \frac{R}{X_L} = -\tan^{-1} \left( \frac{\text{resistance}}{\text{reactance}} \right)$$

**Amplitude:**

$$I = \sqrt{I_L^2 + I_R^2} = U \sqrt{\frac{1}{X_L^2} + \frac{1}{R^2}} = \frac{U}{Z}$$

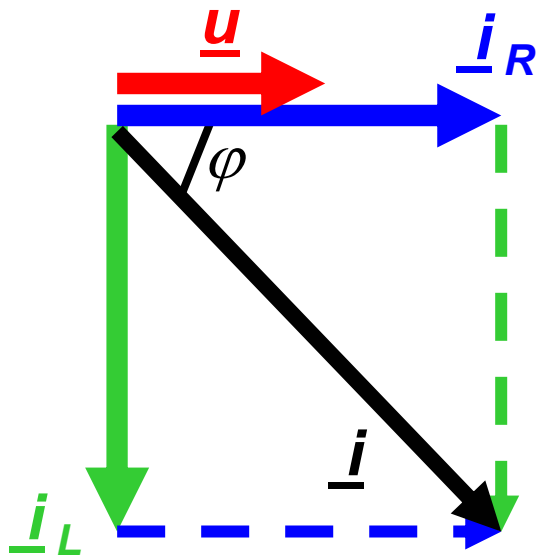**Impedance:**

$$\frac{1}{Z} = \sqrt{\frac{1}{X_L^2} + \frac{1}{R^2}} = \sqrt{\left( \frac{1}{\omega L} \right)^2 + \frac{1}{R^2}}$$



# SUMMARY OF FORMULAE

	D.C.	A.C.
In series	$R = R_1 + R_2$	$Z = \sqrt{R^2 + X^2}$
In parallel	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$	$\frac{1}{Z} = \sqrt{\frac{1}{X^2} + \frac{1}{R^2}}$

## EXAMPLE

D.C.

$$R_1 = 30 \Omega \quad R_2 = 60 \Omega$$

in parallel

$$R = 20 \Omega$$

(33% less than  $R_1$ )

A.C.


$$R = 30 \Omega \quad X = 60 \Omega$$

in parallel

$$Z = 26.8 \Omega$$

(10% less than  $R$ )

## EXAMPLE: LCR CIRCUIT IN PARALLEL

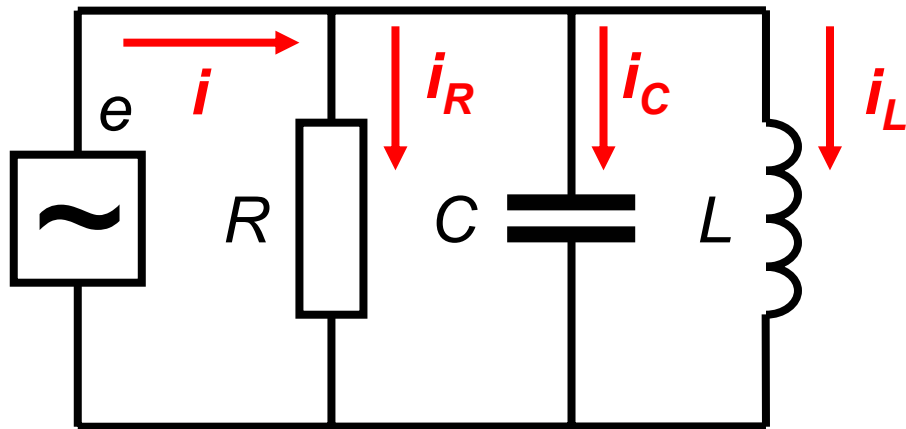

$$I_R = U/R, \quad I_C = U/X_C, \quad I_L = U/X_L$$

$i_R$  in - phase with  $u$ ,

$i_L$  lags  $u$  by  $\pi/2$ ,  $i_C$  leads  $u$  by  $\pi/2$

$$\underline{i} = \underline{i}_R + \underline{i}_C + \underline{i}_L$$

Voltage  $u$  - reference

$$\varphi = \tan^{-1} \frac{I_C - I_L}{I_R} = \tan^{-1} \left[ R \left( \frac{1}{X_C} - \frac{1}{X_L} \right) \right]$$


Amplitude:

$$I = \sqrt{(I_C - I_L)^2 + I_R^2} = U \sqrt{\left( \frac{1}{X_C} - \frac{1}{X_L} \right)^2 + \frac{1}{R^2}} = \frac{U}{Z}$$


$I_L$  and  $I_C$  **may be much larger** than the total current  $I$

Impedance:
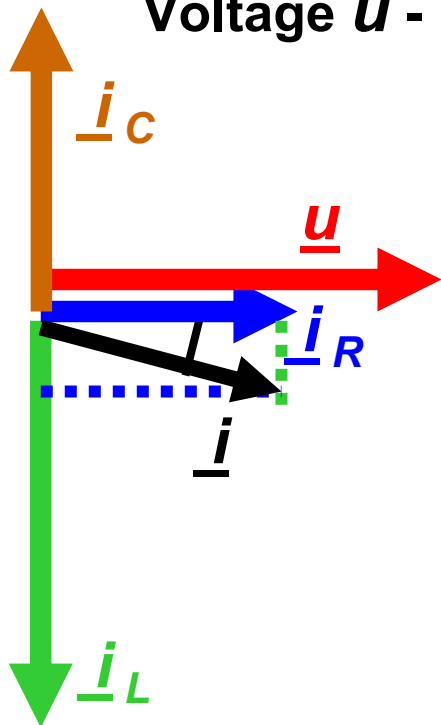
$$\frac{1}{Z} = \sqrt{\left( \frac{1}{X_C} - \frac{1}{X_L} \right)^2 + \frac{1}{R^2}} = \sqrt{\left( \omega C - \frac{1}{\omega L} \right)^2 + \frac{1}{R^2}}$$



# ACTIVE AND REACTIVE CURRENTS

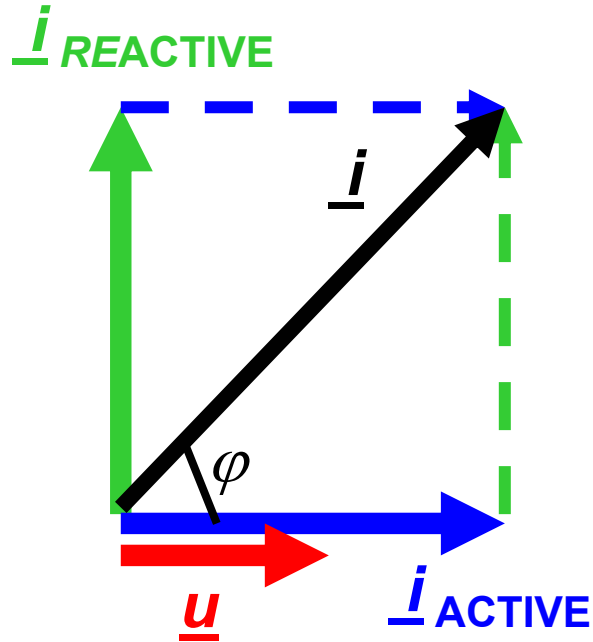

Current in **any** circuit can be represented as a sum of two components:

- 1) in-phase;
- 2) at phase difference of  $90^\circ$  to voltage

In-phase - **active**, or **power** component

$$I_{\text{active}} = I \cos \varphi$$

At  $90^\circ$  to voltage - **reactive**, or **quadrature** component

$$I_{\text{reactive}} = I \sin \varphi$$

$$I^2 = (I_{\text{active}})^2 + (I_{\text{reactive}})^2$$

**RELATION TO ACTIVE POWER:**  $P_{\text{active}} = IU \cos \varphi = I_{\text{active}} U$

$$\text{POWER FACTOR} = \cos \varphi = \frac{I_{\text{active}}}{\sqrt{(I_{\text{active}})^2 + (I_{\text{reactive}})^2}}$$

Resistors are **active**, while capacitors and coils are **reactive** circuit elements

**For purely reactive (capacitive or inductive) circuits, power factor = 0**

# ADMITTANCE, CONDUCTANCE AND SUSCEPTANCE

For D.C. circuits:  $R$  - resistance,  $G=1/R$  - D.C. conductance

For two resistors in parallel:  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad \therefore \quad G = G_1 + G_2$

For A.C. circuits, an equivalent quantity is called **admittance**  $Y$

Admittance =  $\frac{1}{\text{Impedance}}$  :  $Y = \frac{1}{Z} = \frac{I}{U}$  Units - siemens [S]

**A.C. conductance**  $G$  is an **active component** of admittance

A **reactive component** of admittance is called **susceptance** (notation -  $B$ )

$$G = \frac{I_{\text{active}}}{U} \quad B = \frac{I_{\text{reactive}}}{U} \quad \therefore \quad Y = \sqrt{G^2 + B^2}$$

## NOTE

$G$ ,  $B$  and  $Y$  may be conductance, susceptance and admittance, respectively, of circuit elements or of the **whole circuit**

# ADMITTANCE, CONDUCTANCE AND SUSCEPTANCE IMPEDANCE, RESISTANCE AND REACTANCE: THEIR RELATION

$$G = \frac{I_{\text{active}}}{U} = \frac{I_{\text{active}}}{I} \frac{I}{U} = \frac{R}{Z} \cdot \frac{1}{Z} = \frac{R}{Z^2}$$

$$B = \frac{I_{\text{reactive}}}{U} = \frac{I_{\text{reactive}}}{I} \frac{I}{U} = \frac{X}{Z} \cdot \frac{1}{Z} = \frac{X}{Z^2}$$

Note that  $G=1/R$  only for purely resistive circuits

## EXAMPLES


If a resistor  $R_0$  is connected **in series** with a reactive element  $X$ ,  
resistance of the circuit  $R$  is equal to  $R_0$ :  $R = R_0$

However, if a resistor  $R_0$  is connected **in parallel** with a reactive element  $X$ ,  
resistance of the circuit  $R$  is **not** equal to  $R_0$ :  $R \neq R_0$

In this case, **conductance of the circuit**  $G$  is equal to  
conductance of the resistor  $G_0$ :  $G = G_0 = 1/R_0$



## EXAMPLE: MORE COMPLICATED CIRCUIT

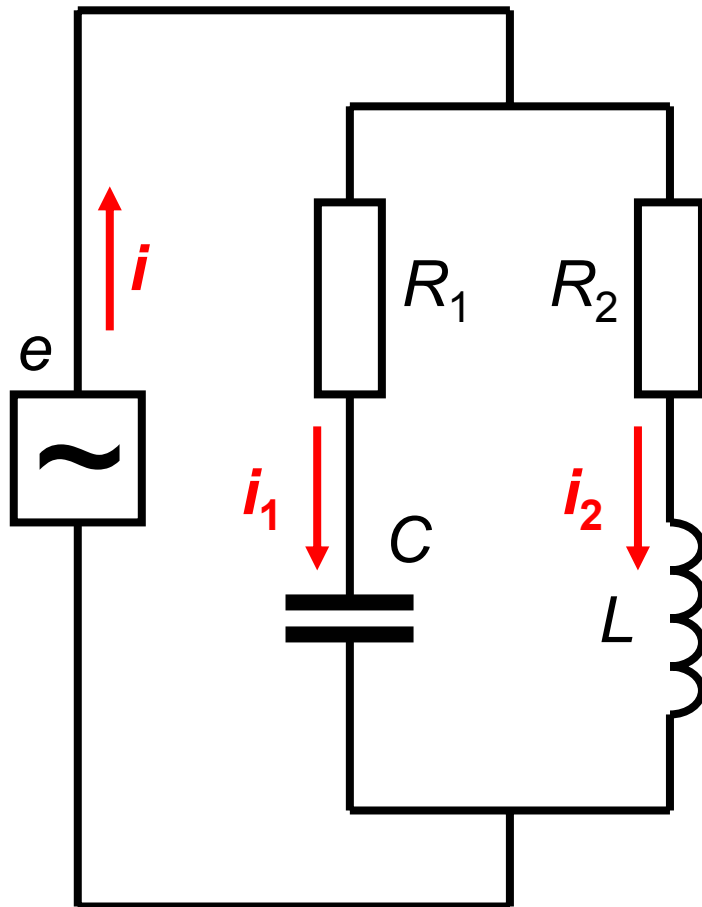


Known parameters:  $e$ , frequency,  $R_1$ ,  $R_2$ ,  $L$ ,  $C$ .


Determine: current, phase angle

### STEP 1

Analysis of the  $R_1C$  segment

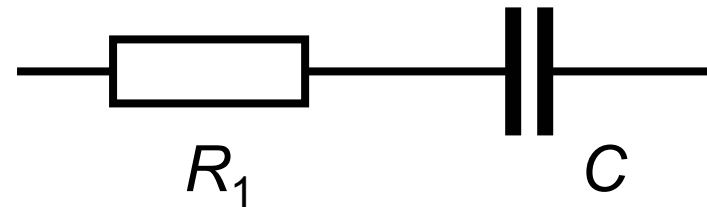


Reference - current  $i_1$

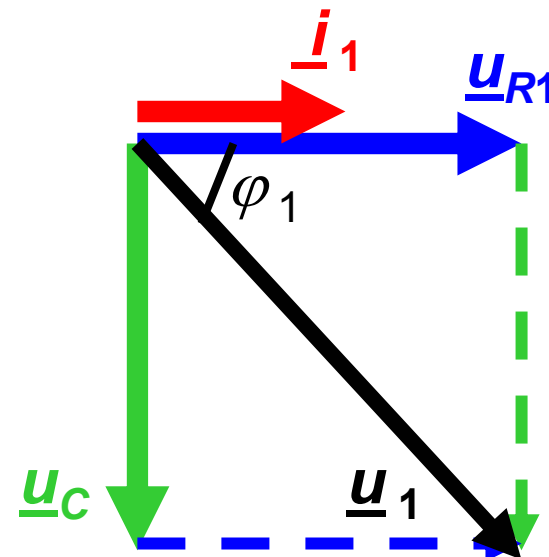


## STEP 2

Analysis of the  $R_2L$  segment

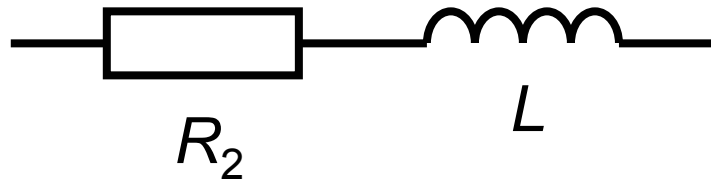


Reference - current  $\underline{i}_2$

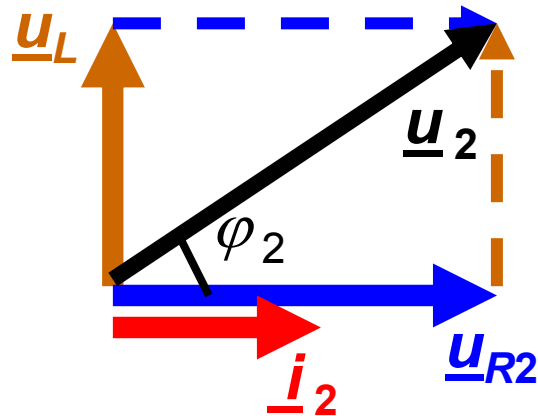
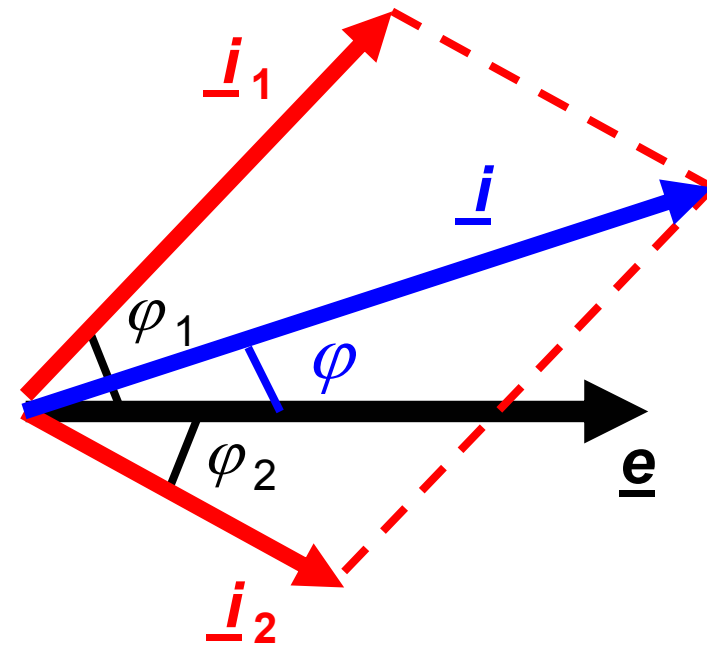
## STEP 3

Analysis of the whole circuit

Reference - voltage  $\underline{u}_1 = \underline{u}_2 = \underline{e}$



For more or less complicated circuits, the method of phasor diagrams becomes rather cumbersome

Anything more efficient?

**Method of complex notations** (next lecture)