

## 9. GENERAL NETWORK THEOREMS

- Main things to learn**
- Superposition theorem
  - Thévenin's theorem
  - Application of the theorems to d.c. and a.c. circuits

The Superposition theorem and the Thévenin's theorem provide an **alternative approach** to analysis of complicated circuits, in particular, circuits with two or more power sources.

These theorems **may be applied both to d.c. and a.c. circuits**  
For a.c. circuits, **complex notations should be used.**

**A circuit must be linear!**

If there is a circuit which contains several power sources and we analyse the circuit basing on Kirchhoff's laws, we need take the power sources into account **simultaneously**.

**Is it possible to consider them separately?**

A circuit which contains one or more power sources is called an **active** circuit, or an **active network**

# SUPERPOSITION THEOREM

**IF**

there is a circuit which contains two or more power sources  
(an active network)

**THEN**

we can find the current in any branch or the potential difference across any branch in the following way:

**1**

We consider the **effect of the first source**, replacing all other sources by resistances equal to their internal resistances


**2**

We **successively** consider the effect of each other source in the same way



**3**

**We add their effects**

# EXAMPLE: D.C. CIRCUIT

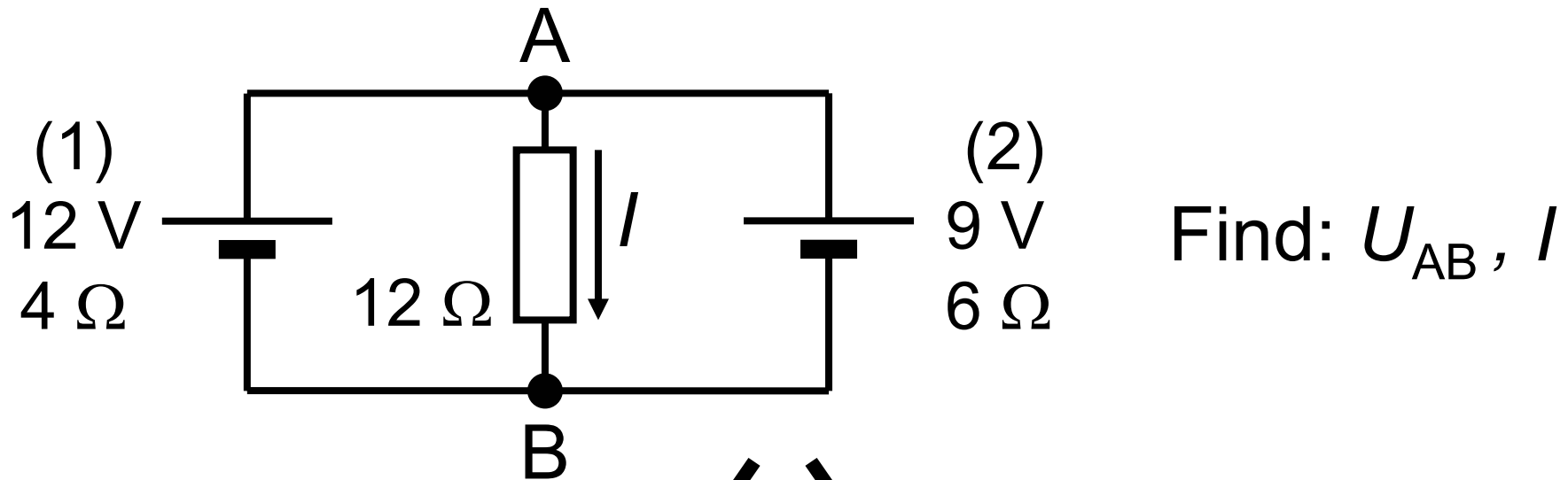


Find:  $U_{AB}$ ,  $I$

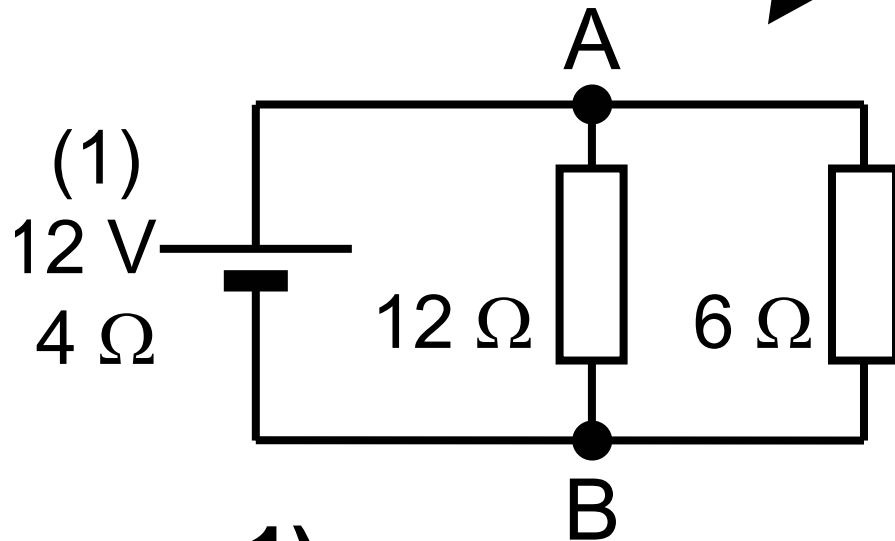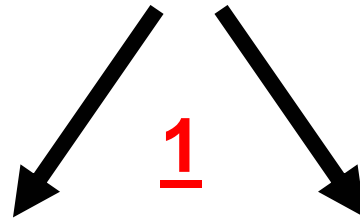

1)


+

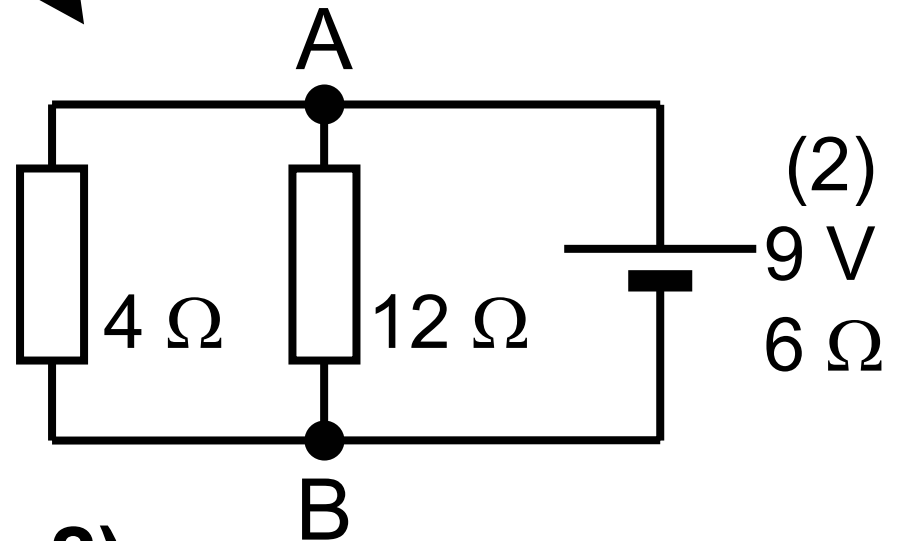

2)

2

Circuit 1) is equivalent to

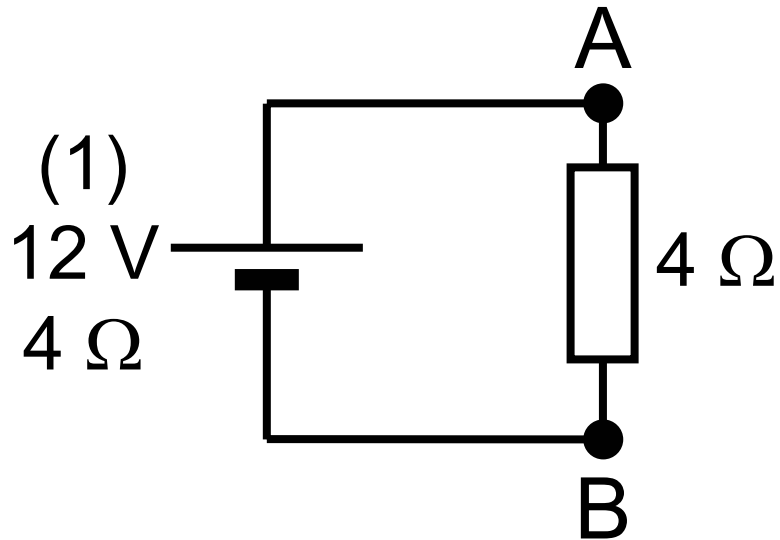


4 Ω is the resistance of the load  
as seen by source (1)

$$I_{(1)} = \frac{12 \text{ V}}{(4 + 4) \Omega} = 1.5 \text{ A}$$

$$U_{AB(1)} = 1.5 \text{ A} \times 4 \Omega = 6 \text{ V}$$

Circuit 2) is equivalent to

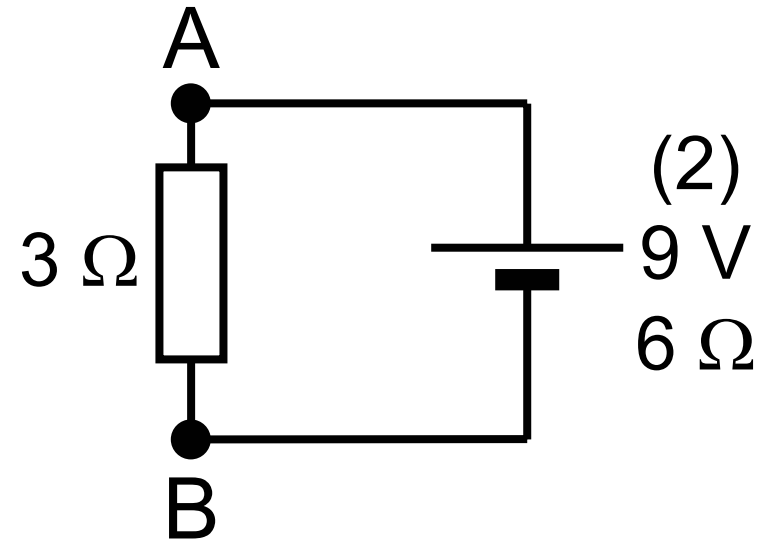

3 Ω is the resistance of the load  
as seen by source (2)


$$I_{(2)} = \frac{9 \text{ V}}{(6 + 3) \Omega} = 1 \text{ A}$$

$$U_{AB(2)} = 1 \text{ A} \times 3 \Omega = 3 \text{ V}$$

3

$$U_{AB} = U_{AB(1)} + U_{AB(2)} = 6 \text{ V} + 3 \text{ V} = 9 \text{ V} \quad ; \quad I = \frac{9 \text{ V}}{12 \Omega} = 0.75 \text{ A}$$


# EXAMPLE: A.C. CIRCUIT

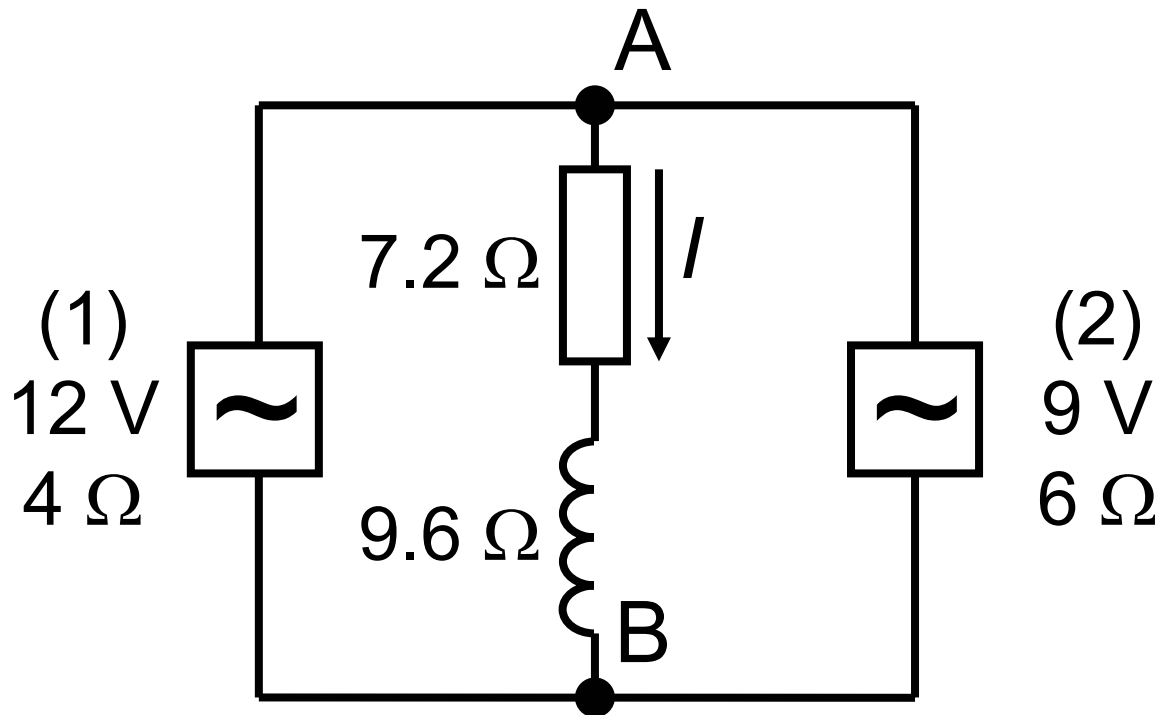


Find:  $U_{AB}$ ,  $I$

Assume that source (2) lags source (1) by  $90^\circ$


Using complex notations:

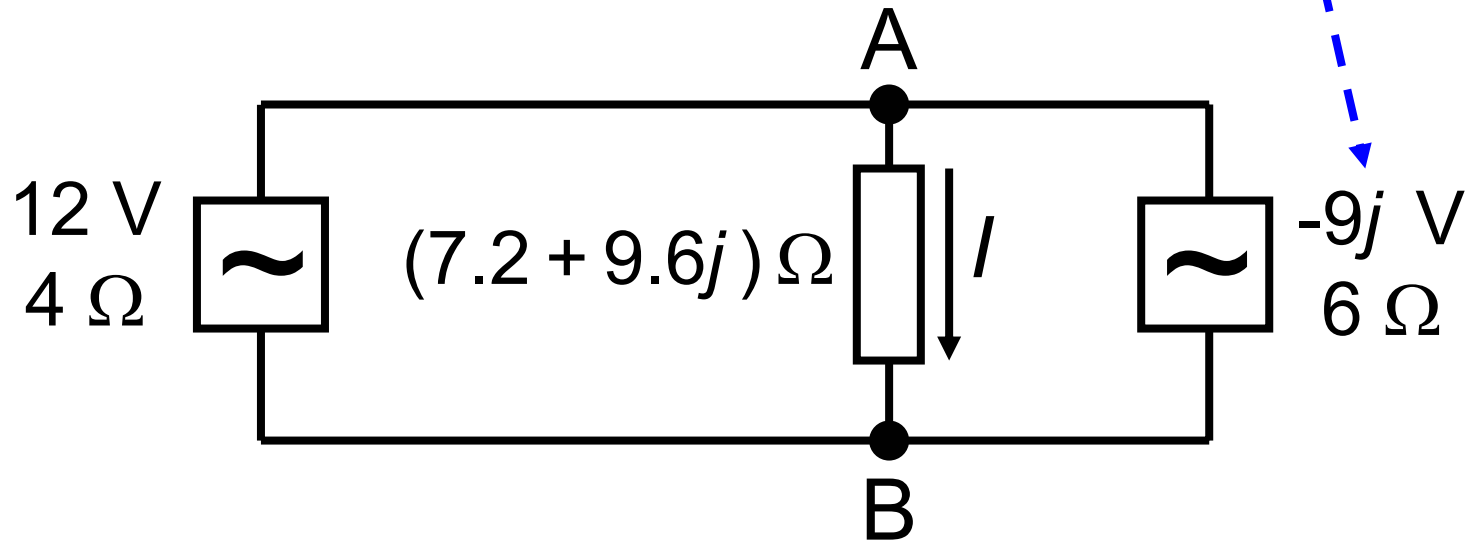

1 THIS IS EQUIVALENT TO

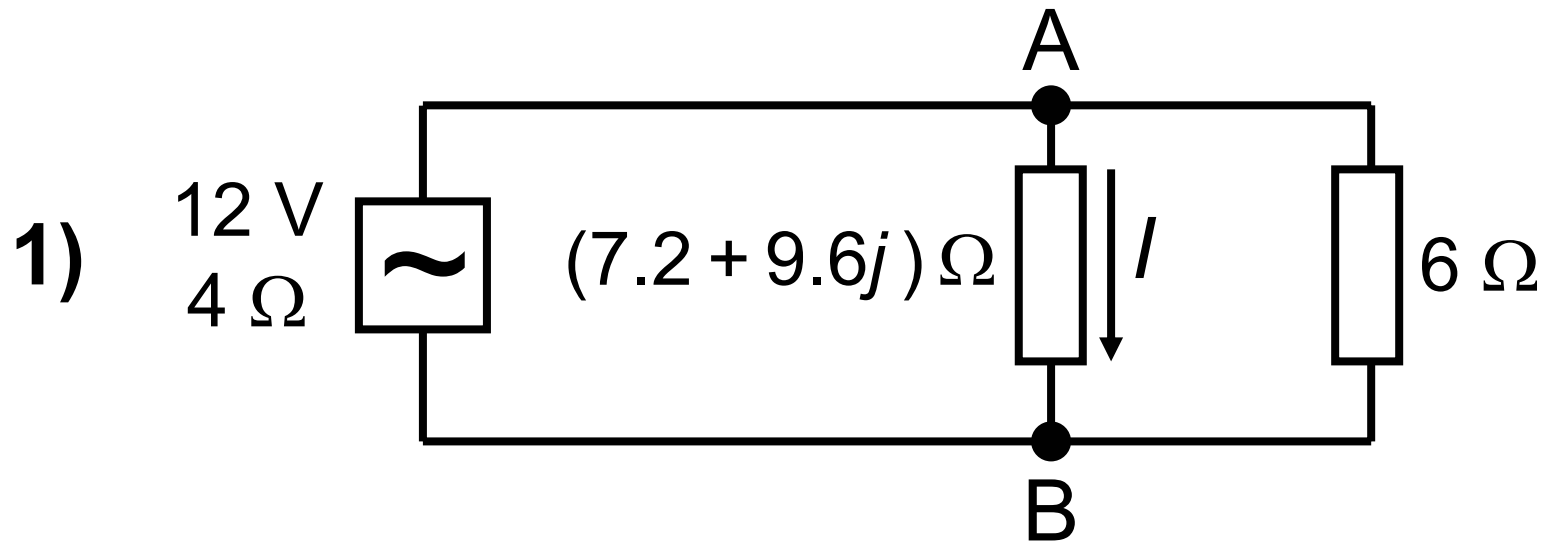


+

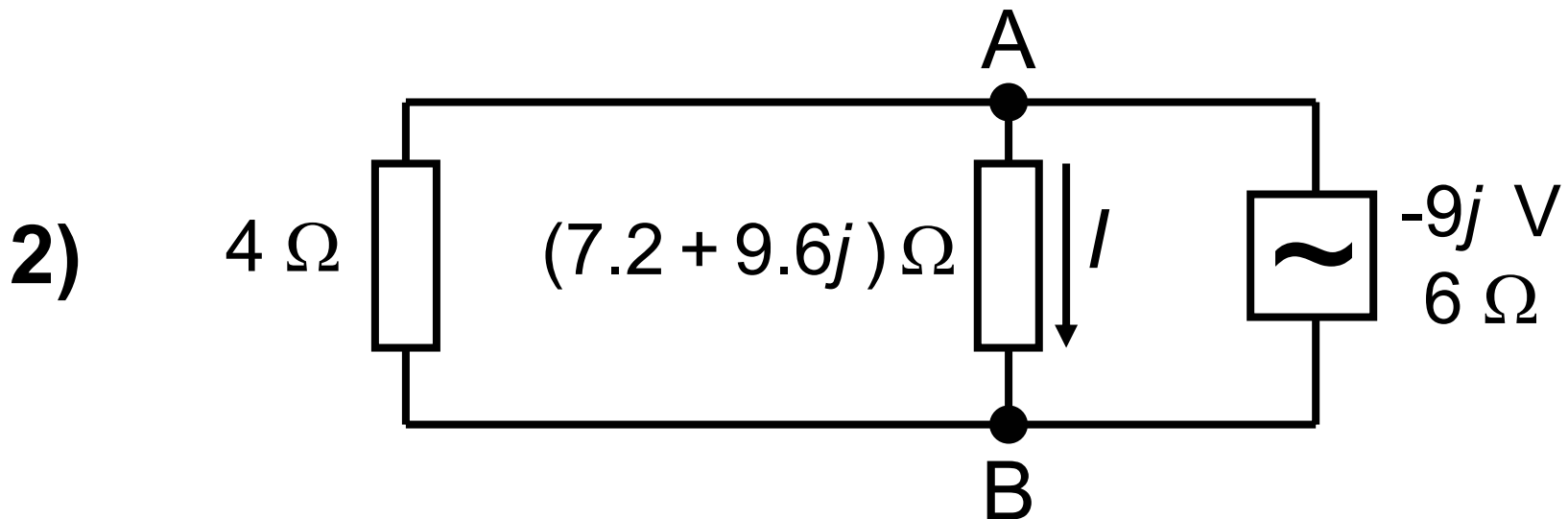


2

Circuit 1) is equivalent to

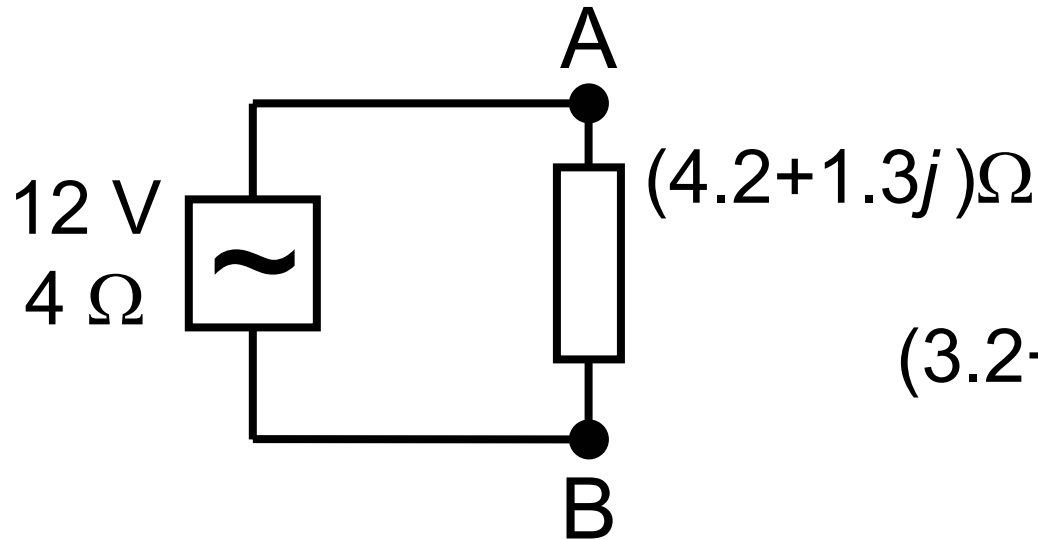

Circuit 2) is equivalent to

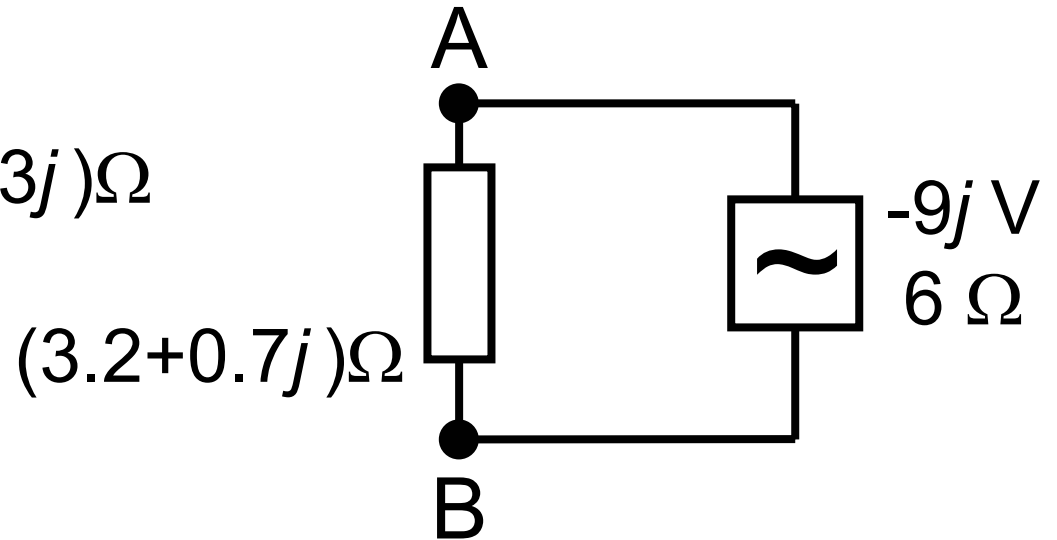

$$I_{(1)} = \frac{12 \text{ V}}{[4 + (4.2 + 1.3j)] \Omega} = (1.4 - 0.2j) \text{ A}$$

$$U_{AB(1)} = (1.4 - 0.2j) \text{ A} \times (4.2 + 1.3j) \Omega = (6.1 + j) \text{ V}$$

$$I_{(2)} = \frac{-9j \text{ V}}{[6 + (3.2 + 0.7j)] \Omega} = (-0.1 - j) \text{ A}$$

$$U_{AB(2)} = (-0.1 - j) \text{ A} \times (3.2 + 0.7j) \Omega = (0.4 - 3.3j) \text{ V}$$

### **3** FINAL RESULT

$$U_{AB} = U_{AB(1)} + U_{AB(2)} = (6.1 + j) \text{ V} + (0.4 - 3.3j) \text{ V} = (6.5 - 2.3j) \text{ V}$$

$$I = \frac{(6.5 - 2.3j) \text{ V}}{(7.2 + 9.6j) \Omega} = (0.17 - 0.55j) \text{ A}$$

#### **Amplitude**

$$|U_{AB}| = |6.5 - 2.3j| = \sqrt{6.5^2 + 2.3^2} = 6.9 \text{ V}$$

$$|I| = |0.17 - 0.55j| = \sqrt{0.17^2 + 0.55^2} = 0.57 \text{ A}$$

#### **Phase**

If the phase of the source (1) is taken as reference (zero), phases are:

$$\text{for } U_{AB} : \varphi = \tan^{-1}(-2.3 / 6.5) = -19^\circ$$


(voltage  $U_{AB}$  lags the voltage from the source (1) by  $19^\circ$ )

$$\text{for } I : \varphi = \tan^{-1}(-0.55 / 0.17) = -73^\circ$$

(current  $I$  lags the voltage from the source (1) by  $73^\circ$ )



# THÉVENIN'S THEOREM

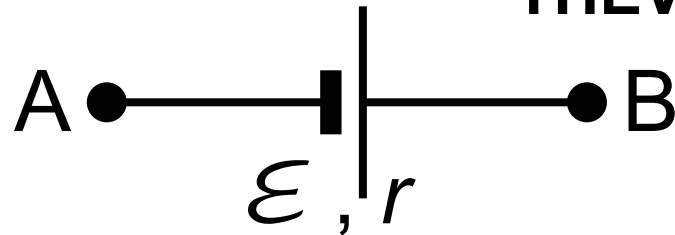

Any battery can be characterised by two parameters:


- 1) EMF  $\mathcal{E}$  ; 2) internal resistance  $r$

The EMF  $\mathcal{E}$  equals the open-circuit voltage between the terminals A and B;  $r$  equals the ratio of  $\mathcal{E}$  to the current if the terminals A and B are short-circuited

## Thévenin's theorem


**Any active circuit (network) having terminals A and B is equivalent and can be replaced by a constant-voltage source which has an EMF  $\mathcal{E}$  and an internal resistance  $r$ .**

Another formulation:

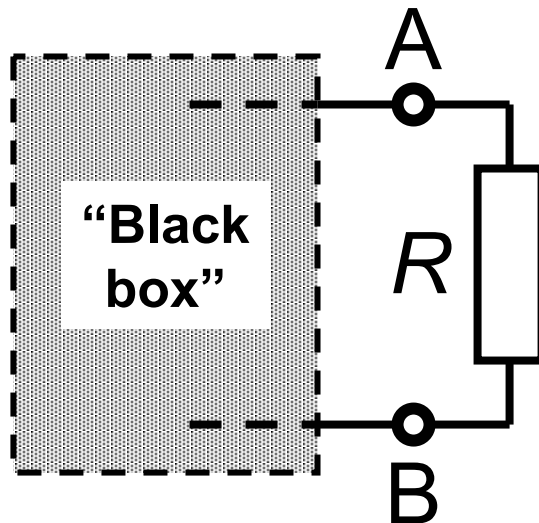

The current through a resistor  $R$  connected across any two points A and B of an active network can be obtained by dividing the potential difference between A and B, with  $R$  disconnected, by  $(R + r)$  where  $r$  is the resistance of the network measured between points A and B with  $R$  disconnected and the sources of EMF replaced by their internal resistances.

## EXAMPLE

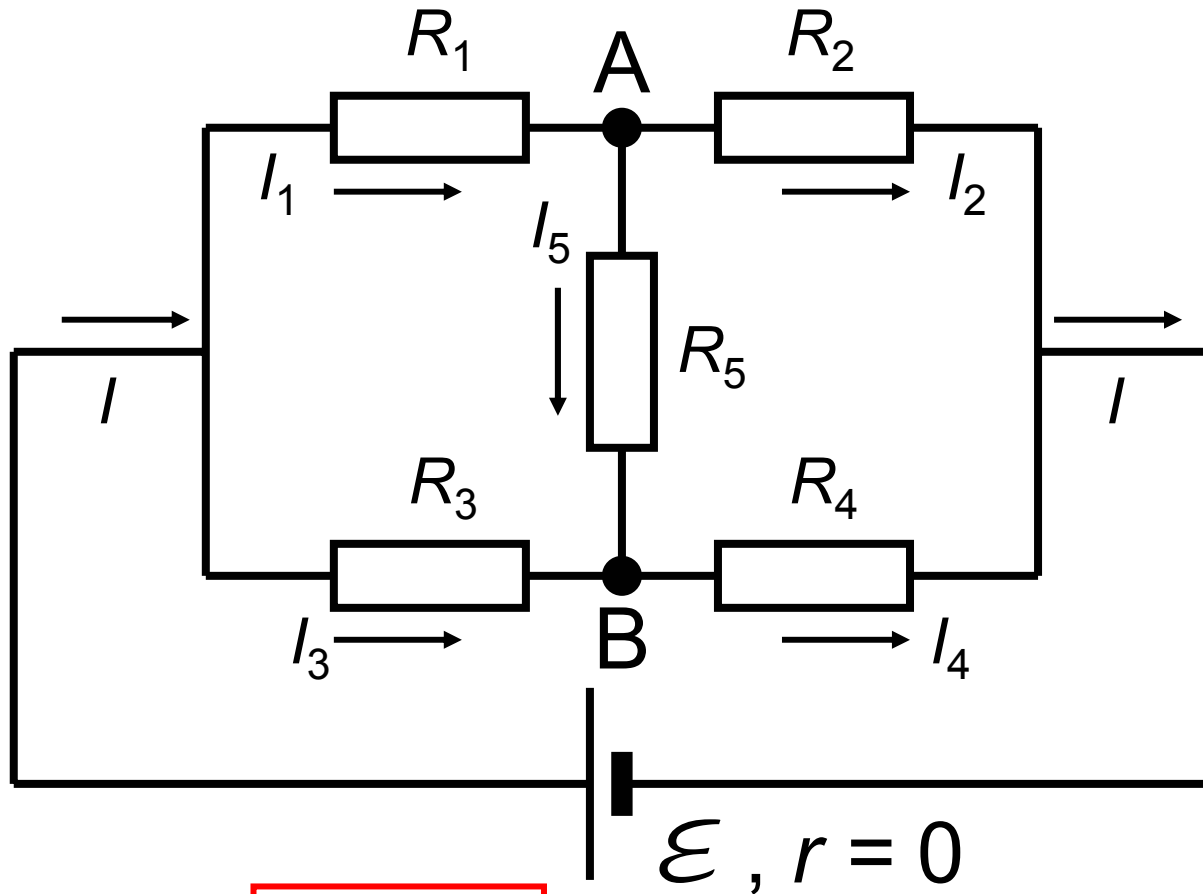

$$\mathcal{E} = 24 \text{ V}$$

$$R_1 = 14 \ \Omega$$

$$R_2 = 42 \ \Omega$$

$$R_3 = 48 \ \Omega$$

$$R_4 = 24 \ \Omega$$

$$R_5 = 13.5 \ \Omega$$

Find:  $U_{AB}$ ,  $I_5$

$$U_1 = I_1 R_1$$

$$U_2 = I_2 R_2$$

$$U_3 = I_3 R_3$$

$$U_4 = I_4 R_4$$

$$U_5 = I_5 R_5$$

$$-I_1 + I_2 + I_5 = 0$$

$$-I_3 + I_4 - I_5 = 0$$

$$I = I_1 + I_3$$

$$R = \frac{\mathcal{E}}{I}$$

$$U_1 + U_2 = \mathcal{E}$$

$$U_3 + U_4 = \mathcal{E}$$

$$U_1 + U_5 + U_4 = \mathcal{E}$$

# USING THE THÉVENIN'S THEOREM


**1**

Determine  $U_{AB}^*$  when  $R_5$  is disconnected

$$U_{CA} = 6 \text{ V}; U_{AD} = 18 \text{ V}$$

$$U_{CB} = 16 \text{ V}; U_{BD} = 8 \text{ V}$$
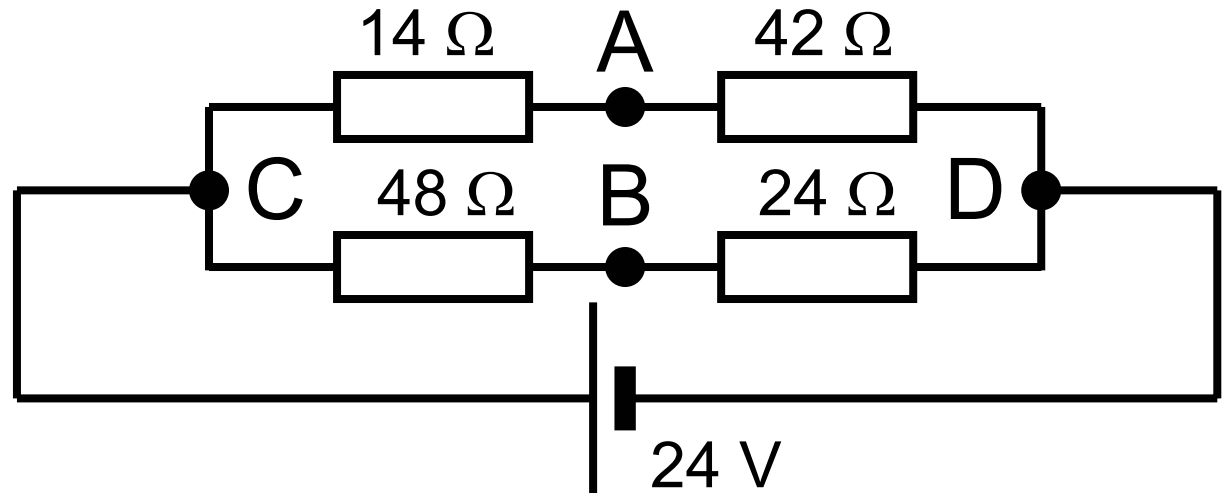
$$U_{AB}^* = -U_{CA} + U_{CB} = 10 \text{ V}$$




**2**

Determine  $r_{AB}^*$  when  $R_5$  is disconnected and the battery is replaced by equivalent (zero) resistance

$$\frac{1}{R_{AC}} = \frac{1}{14 \Omega} + \frac{1}{42 \Omega} \quad \therefore R_{AC} = 10.5 \Omega$$

$$\frac{1}{R_{CB}} = \frac{1}{48 \Omega} + \frac{1}{24 \Omega} \quad \therefore R_{CB} = 16 \Omega$$
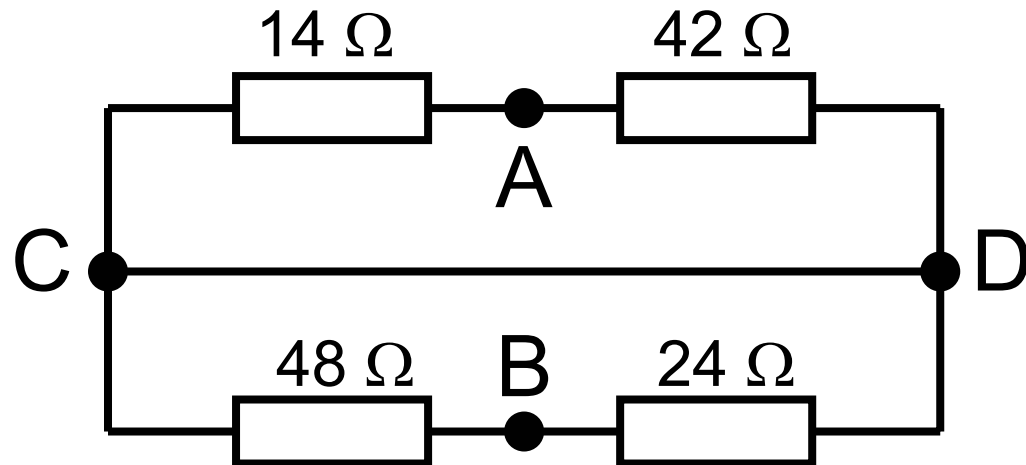
$$\therefore r_{AB}^* = 10.5 + 16 = 26.5 \Omega$$



## FINAL RESULT

3

Determine current  $I_5$  which flows through  $R_5$

$$I_5 = \frac{U_{AB}^*}{R_5 + r_{AB}^*} = \frac{10 \text{ V}}{13.5 \Omega + 26.5 \Omega} = \frac{10 \text{ V}}{40 \Omega} = 0.25 \text{ A}$$

Determine voltage  $U_{AB}$

$$U_{AB} = I_5 \times R_5 = 0.25 \text{ A} \times 13.5 \Omega = 3.4 \text{ V}$$

**In the same way the Thévenin's theorem can be applied to a.c. circuits.**

**Complex notations should be used.**

**The circuit must be linear !!!**